

# EED2003 Digital Design

## Presentation 2: Boolean Algebra

Asst. Prof.Dr. Ahmet ÖZKURT  
Asst. Prof.Dr Hakkı T. YALAZAN

Based on the Lecture Notes by Jaeyoung Choi [choi@comp.ssu.ac.kr](mailto:choi@comp.ssu.ac.kr) Fall 2000

## 2.1 Binary Logic and Gates

- Digital circuits
  - hardware components that manipulate binary information
  - implemented using transistors and interconnections in IC
  - each basic circuit is called *logic gate*
    - performs a specific logical operation
- Boolean Algebra
  - mathematical notation to specify the operation of each gate
  - used to analyze and design circuits

## 2.1 Binary Logic and Gates

- Binary Logic

- take on two discrete values & with the operations of mathematical logic

- three logical operations

1) AND             $Z = X \cdot Y$         (Z is equal to X and Y)

2) OR             $Z = X + Y$         (Z is equal to X or Y)

3) NOT            $Z = X'$             (Z is equal to NOT X)

-- complement operation ( $0 \Rightarrow 1$  &  $1 \Rightarrow 0$ )

- AND/OR is similar to multiplication/addition

## 2.1 Binary Logic and Gates

- logical OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

- logical AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 1 = 1$$

- logical NOT

$$0' = 1$$

$$1' = 0$$

AND

X	Y	$X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR



X	Y	$X+Y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT

X	$X'$
0	1
1	0
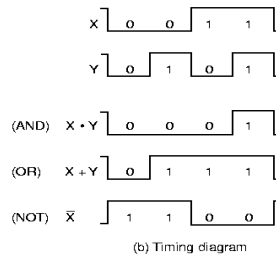 
## 2.1 Binary Logic and Gates

- Logic Gates
  - electronic circuits that operate on one or more input signals to produce an output signal
  - voltage operated circuits: logic 0 & logic 1
  - intermediate region is crossed during state *transition*



## 2.2 Boolean Algebra

- deal with binary variables and logic operations
  - with three basic logic operations AND, OR, NOT
  - express logical relationship between binary variables
- Consider  $F = X + Y' Z$ 
  - represented in a truth table
  - transformed from an algebraic expression into a circuit diagram composed of logic gates (Fig 2.3)

$$F = X + Y' Z$$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

## 2.2 Boolean Algebra

- Basic Identities of Boolean Algebra
  - most basic identities of Boolean algebra
  - *dual* - obtained by interchanging OR and AND, and replacing 1's by 0's and 0's by 1's

1. $X + 0 = X$	2. $X \cdot 1 = X$	
3. $X + 1 = 1$	4. $X \cdot 0 = 0$	
5. $X + X = X$	6. $X \cdot X = X$	
7. $X + \bar{X} = 1$	8. $X \cdot \bar{X} = 0$	
9. $\overline{\bar{X}} = X$		
10. $X + Y = Y + X$	11. $XY = YX$	Commutative
12. $X + (Y + Z) = (X + Y) + Z$	13. $X(YZ) = (XY)Z$	Associative
14. $X(Y + Z) = XY + XZ$	15. $X + YZ = (X + Y)(X + Z)$	Distributive
16. $\overline{X + Y} = \bar{X} \cdot \bar{Y}$	17. $\overline{X \cdot Y} = \bar{X} + \bar{Y}$	DeMorgan's

Table 2-3. Basic Identities of Boolean Algebra


## 2.2 Boolean Algebra

- $AB + C + 1 = 1$  (by identity 3)
- commutative laws -- the order doesn't affect the result
  - $X + Y = Y + X,$
  - $XY = YX$
- associative laws -- parentheses can be removed altogether
  - $X + (Y + Z) = (X + Y) + Z = X + Y + Z$
  - $X(YZ) = (XY)Z = X Y Z$
- distributive laws (dual)
  - $X + YZ = (X + Y)(X + Z)$
  - $(A + B)(A + CD) = ?$
- DeMorgan's theorem -- obtain complement of an expression
  - $(X + Y)' = X' Y'$     $(XY)' = X' + Y'$ 
    - can be extended to three or more variables
    - $(A + B + C + \dots)' = A' B' C' \dots$

## 2.2 Boolean Algebra
 
### ■ Algebraic Manipulation

- Boolean algebra is a useful tool for simplifying digital circuits
- $F = X'YZ + X'YZ' + XZ$   
 $= X'Y(Z+Z') + XZ$   
 $= X'Y \cdot 1 + XZ$   
 $= X'Y + XZ$
- compare two implementations in Fig 2.4



## 2.2 Boolean Algebra

- use truth table to verify two expressions (Table 2.5)
- manipulate Boolean algebra  $\implies$  obtain a simpler circuit
- popular tools
  1.  $X + XY = X(1 + Y) = X$
  2.  $XY + XY' = X(Y + Y') = X$
  3.  $X + X'Y = (X + X')(X + Y) = X + Y$
  4.  $X(X + Y) = X + XY = X(1 + Y) = X$
  5.  $(X + Y)(X + Y') = X + YY' = X$
  6.  $X(X' + Y) = XX' + XY = XY$
- consensus theorem
  - $XY + X'Z + YZ = XY + X'Z$  (prove it!)
  - dual  $(X+Y)(X'+Z)(Y+Z) = (X+Y)(X'+Z)$

$$\begin{aligned} \text{(Ex)} \quad (A+B)(A'+C) &= AA' + AC + A'B + BC \\ &= AC + A'B + BC = AC + A'B \end{aligned}$$



## 2.2 Boolean Algebra

- Complement of a Function
  - obtained from an interchange of 1's to 0's and 0's to 1's
  - derived algebraically by applying DeMorgan's theorem

(Ex 2.1) Find the complement of  $F1 = X'YZ' + X'Y'Z$

$$\begin{aligned}F1' &= (X'YZ' + X'Y'Z)' \\ &= (X'YZ')' (X'Y'Z)' \\ &= (X + Y' + Z) (X + Y + Z')\end{aligned}$$

(Ex 2.2) Find the complement of  $F1 = X'YZ' + X'Y'Z$   
by taking dual and complementing each literal

dual of F1	$(X' + Y + Z') (X' + Y' + Z)$
comp of each literal	$(X + Y' + Z) (X + Y + Z')$



## 2.3 Standard Forms

- facilitate the simplification procedures for Boolean expression
- contain product terms ( $XY'Z$ ) and sum terms ( $X+Y+Z'$ )
- Minterms & Maxterms
  - minterm (a product term) & maxterm (a sum term)
  - all the variables appear exactly once
  - show exactly one combination of the binary variables in a truth table
  - $2^n$  distinct terms for n variables

(Ex) 4 minterms for 2 variables X & Y

$$X'Y', X'Y, XY', \& XY$$

## 2.3 Standard Forms

X	Y	Z	Product Term	Symbol	$m_0$	$m_1$	$m_2$	$m_3$	$m_4$	$m_5$	$m_6$	$m_7$
0	0	0	$\overline{X}\overline{Y}\overline{Z}$	$m_0$	1	0	0	0	0	0	0	0
0	0	1	$\overline{X}\overline{Y}Z$	$m_1$	0	1	0	0	0	0	0	0
0	1	0	$\overline{X}Y\overline{Z}$	$m_2$	0	0	1	0	0	0	0	0
0	1	1	$\overline{X}YZ$	$m_3$	0	0	0	1	0	0	0	0
1	0	0	$X\overline{Y}\overline{Z}$	$m_4$	0	0	0	0	1	0	0	0
1	0	1	$X\overline{Y}Z$	$m_5$	0	0	0	0	0	1	0	0
1	1	0	$XY\overline{Z}$	$m_6$	0	0	0	0	0	0	1	0
1	1	1	$XYZ$	$m_7$	0	0	0	0	0	0	0	1

X	Y	Z	Sum Term	Symbol	$M_0$	$M_1$	$M_2$	$M_3$	$M_4$	$M_5$	$M_6$	$M_7$
0	0	0	$X + Y + Z$	$M_0$	0	1	1	1	1	1	1	1
0	0	1	$X + Y + \overline{Z}$	$M_1$	1	0	1	1	1	1	1	1
0	1	0	$X + \overline{Y} + Z$	$M_2$	1	1	0	1	1	1	1	1
0	1	1	$X + \overline{Y} + \overline{Z}$	$M_3$	1	1	1	0	1	1	1	1
1	0	0	$\overline{X} + Y + Z$	$M_4$	1	1	1	1	0	1	1	1
1	0	1	$\overline{X} + Y + \overline{Z}$	$M_5$	1	1	1	1	1	0	1	1
1	1	0	$\overline{X} + \overline{Y} + Z$	$M_6$	1	1	1	1	1	1	0	1
1	1	1	$\overline{X} + \overline{Y} + \overline{Z}$	$M_7$	1	1	1	1	1	1	1	0

es

## 2.3 Standard Forms

- $m_j$  (minterm) -- complemented if the bit is 0  
uncomplemented if the bit is 1
- $M_j$  (maxterm) -- complemented if the bit is 1  
uncomplemented if the bit is 0
  - $j$  denotes the binary number of the term
- minterm: having the minimum No of 1's in its truth table  
maxterm: having the maximum No of 1's in its truth table
- a minterm and maxterm with the same subscript are complements of each other ( $M_j = m_j'$ )

(Ex)  $(m_3)' = (\overline{X}' Y Z)' = X + Y' + Z' = M_3$

## 2.3 Standard Forms

- a Boolean function can be expressed by a *sum of minterms*

(Ex) Table 2-8(a)

$$F = X'Y'Z' + X'YZ' + XY'Z + XYZ = m_0 + m_2 + m_5 + m_7$$

$$F(X, Y, Z) = \sum m(0, 2, 5, 7) \quad (\Sigma = \text{logical sum, Boolean OR})$$

$$F' = X'YZ + X'YZ' + XY'Z' + XYZ' = m_1 + m_3 + m_4 + m_6$$

$$F(X, Y, Z)' = \sum m(1, 3, 4, 6)$$

$$F = (m_1 + m_3 + m_4 + m_6)' = m_1' \cdot m_3' \cdot m_4' \cdot m_6'$$

$$= M_1 \cdot M_3 \cdot M_4 \cdot M_6$$

$$= (X + Y + Z') \cdot (X + Y' + Z') \cdot (X' + Y + Z) \cdot (X' + Y' + Z)$$

$$F(X, Y, Z) = \Pi M(1, 3, 4, 6) \quad (\Pi: \text{logical product, Boolean AND})$$

- summary of minterms (p46)
- a function can be converted to the sum of minterms form by means of a truth table

## 2. 3 Standard Forms

(Ex)  $E = Y' + X'Z'$

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

from the truth table,

$$E(X, Y, Z) = \sum m(0, 1, 2, 4, 5)$$

$$E(X, Y, Z)' = \sum m(3, 6, 7)$$

(the total number of minterms in E and E' is 8)




## 2.3 Standard Forms

- Sum of Products

- a standard algebraic expression
- obtained directly from a truth table (sum of minterms) & simplify the expression to *sum-of-products* form

(Ex)  $F = Y' + X'YZ' + XY$

 three product terms -- two AND gates, one OR gate  
two-level implementation




## 2.3 Standard Forms

(Ex)  $F = AB + C(D+E)$  (three-level)

$\Rightarrow AB + CD + DE$  (two-level)

 two-level implementation is preferred for its delay time




## 2.3 Standard Forms

- Product of Sums
  - another standard algebraic expression
  - obtained by forming a logical product of sum terms

(Ex)  $F = X(Y'+Z)(X+Y+Z')$

needs 2 OR gates and one AND gates

 



## 2.4 Map Simplification

- Karnough map (K-map)
  - to simplify Boolean functions of up to 4 variables  
(5 or 6 variables can be drawn, but cumbersome to use)
  - a diagram of squares, each representing one minterm
  - simplified expressions are in sum-of-products or product-of-sums
    - two-level implementations
  
## 2.4 Map Simplification

- Two-Variable Map

- four minterms for a Boolean function with 2 variables




$$m_1+m_2+m_3 = X'Y+XY'+XY = X+Y$$

(by algebra)  $\Rightarrow X'Y+X(Y'+Y) = X'Y+Y$


## 2.4 Map Simplification

- Three-variable Map

- 8 minterms for 3 variables



 


Ex2.3  $F(X,Y,Z) = \sum m(2,3,4,5)$

 



(from K-map)  $F = X'Y + XY'$

## 2.4 Map Simplification

   

  
## 2.4 Map Simplification

Ex2.4  $F_1(X,Y,Z) = \sum m(3,4,6,7)$        $F_2(X,Y,Z) = \sum m(0,2,4,5,6)$



(Ex)

 

$$F_2(X,Y,Z) = \sum m(1,3,4,5,6)$$

$$= X'Z + XZ' + XY'$$


$$\text{or } = X'Z + XZ' + YZ$$

## 2.4 Map Simplification


- Four-variable Map
  - 16 minterms for 4 variables

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$
$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$m_8$	$m_9$	$m_{11}$	$m_{10}$


(a)

 

(b)

 

(a)

 

(b)

## 2.4 Map Simplification

Ex2.5  $F(W,X,Y,Z)$   
 $= \sum m(0,1,2,4,5,6,8,9,12,13,14)$

$$F = Y' + W'Z' + XZ'$$

	YZ	00	01	11	10
WX	00	1	1		1
	01	1	1		1
	11	1	1		1
	10	1	1		

Ex2.6  $F = A'B'C' + B'CD' + A'BCD' + AB'C'$

$$F = B'D' + B'C' + A'CD'$$

	CD	00	01	11	10
AB	00	1	1		1
	01				1
	11				
	10	1	1		1

## 2.5 Map Manipulation

- ensure that all minterms of the functions are included
- necessary to minimize the number of terms
  
- Essential Prime Implicants
  - *implicant*
    - if the function has the value 1 for all minterms of the product term
  - *prime implicant*
    - if the removal of any literal from an implicant results in a product term that is not an implicant
    - a product term obtained by combining the maximum possible number of adjacent squares in the map
  - *essential prime implicant*
    - if a minterm of a function is included in only one prime implicant

## 2.5 Map Manipulation

- To find the simplified expression from the map,
  - 1) first determine all prime implicant
  - 2) simplified expression
  - all the essential prime implicant + other prime implicant

(Ex) Fig 2.21

		CD			
		00	01	11	10
AB	00		1	1	
	01	1	1	1	1
	11	1			1
	10				

A'D and BD': essential  
 prime implicants  
 A'B: not essential

## 2.5 Map Manipulation

(Ex) Fig 2.22

		CD			
		00	01	11	10
AB	00	1			
	01		1		
	11	1	1	1	
	10			1	1

$A'B'C'D'$ ,  $BC'D$ ,  $ABC'$ ,  $AB'C$ : essential prime implicants

$ACD$  or  $ABD$ : not essential

$$F = A'B'C'D' + BC'D + ABC' + AB'C + ACD \text{ or } ABD$$

## 2.5 Map Manipulation

- Nonessential Prime Implicant
  - Selection Rule
    - minimize the overlap among prime implicant as much as possible

Ex2.7  $F(A,B,C,D) = \Sigma m(0,1,2,4,5,10,11,13,15)$

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	1	1	0	0
	11	0	1	1	0
	10	0	0	1	1

$$F' = A'C' + ABD + AB'C + A'B'D'$$

## 2.5 Map Manipulation

- Product-of-Sums Simplification
  - from sum-of-products to product-of-sums
  - complement the function (taking a dual)
    - 1) Combine the squares marked with 0's
    - 2) change the function,
      - which is expressed in product of sums to sum of products

Ex2.8  $F(A,B,C,D) = \Sigma m(0,1,2,5,8,9,10)$

		CD			
		00	01	11	10
	AB				
	00	1	1	0	1
	01	0	1	0	0
	11	0	0	0	0
	10	1	1	0	1

$$F' = AB + CD + BD'$$

$$F = (A'+B')(C'+D')(B'+D)$$

## 2.5 Map Manipulation

Ex)  $F = (A'+B'+C)(B + D)$

- 1) plot the map by taking its complement
  - $F' = ABC' + B'D'$
- 2) marking 0's in the squares to represent  $F'$ 
  - remaining squares are marked with 1's
- 3) combine the 0's and then complement the function

- Don't Care Conditions
  - unspecified minterms of a function
  - ex) 4-bit binary code for the decimal digits
  - marked with cross (X)
  - provide the further simplification of the function



## 2.5 Map Manipulation

Ex)  $F(A,B,C,D) = \Sigma m(1,3,7,11,15)$

$d(A,B,C,D) = \Sigma m(0,2,5)$

	CD	00	01	11	10
AB					
00		X	1	1	X
01		0	X	1	0
11		0	0	1	0
10		0	0	1	0

$F = CD + A'B' = CD + A'D$

obtain a simplified product-

	CD	00	01	11	10
AB					
00		X	1	1	X
01		0	X	1	0
11		0	0	1	0
10		0	0	1	0

$F' = Z' + WY'$

$F = Z(W' + Y)$

## 2.6 NAND and NOR Gates




- Boolean functions are expressed in terms of AND, OR, NOT
- straight forward to implement the function with these gates
- Other useful logic gates

Name	Distinctive shape	Rectangular shape	Algebraic equation	Truth table															
AND			$F = XY$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	X	Y	F	0	0	0	0	1	0	1	0	0	1	1	1
X	Y	F																	
0	0	0																	
0	1	0																	
1	0	0																	
1	1	1																	
OR			$F = X + Y$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	1
X	Y	F																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	
NOT (inverter)			$F = \bar{X}$	<table border="1"> <tr><td>X</td><td>F</td></tr> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </table>	X	F	0	1	1	0									
X	F																		
0	1																		
1	0																		
Buffer			$F = X$	<table border="1"> <tr><td>X</td><td>F</td></tr> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </table>	X	F	0	0	1	1									
X	F																		
0	0																		
1	1																		
NAND			$F = \overline{XY}$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	X	Y	F	0	0	1	0	1	1	1	0	1	1	1	0
X	Y	F																	
0	0	1																	
0	1	1																	
1	0	1																	
1	1	0																	
NOR			$F = \overline{X + Y}$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	0
X	Y	F																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	0																	
Exclusive-OR (XOR)			$F = XY + \bar{X}\bar{Y}$ $= X \oplus Y$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	0
X	Y	F																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	0																	
Exclusive-NOR (XNOR)			$F = XY + \bar{X}\bar{Y}$ $= X \oplus \bar{Y}$	<table border="1"> <tr><td>X</td><td>Y</td><td>F</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	1
X	Y	F																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	1																	
   
## 2.6 NAND and NOR Gates




- NAND gate

- a universal gate
  - because any digital system can be implemented with it



- Implementation of NOT (inverter), AND, OR

   - 2 graphic symbols: AND-invert & invert-OR





## 2.6 NAND and NOR Gates


- Two-Level Implementation

- easy to implement with NAND gates, if the function is in sum of products form

(Ex)  $F = AB + CD$

  


$$F = ((AB)'(CD)')' = AB + CD$$

 


(c)
 
## 2.6 NAND and NOR Gates


Ex2.9)  $F(X,Y,Z) = \Sigma m(1,2,3,4,5,7)$



(a)

 

(b)

 

(c)


## 2.6 NAND and NOR Gates

### ■ Multilevel NAND Circuits


□ with three or more levels

- 1) convert all AND gates to NAND gates w/ AND-invert
- 2) convert all OR gates to NAND gates w/ invert-OR
- 3) convert rest small circles to inverters

Ex)  $F = A(CD + B) + BC'$

 




(a) AND - OR gates

 

  
 
## 2.6 NAND and NOR Gates

- NOR gate

- dual of the NAND operation
- another universal gate
- implementation of NOT (inverter), AND, OR



- two graphic symbol for NOR gate

  


## 2.6 NAND and NOR Gates


- Two-Level Implementation

- easy to implement with NOR gates, if the function is in product of sums form

(Ex)  $F = (A + B) (C + D) E$

 

(Ex)  $F = (AB' + A'B) E (C + D')$

 

## 2.7 Exclusive-OR Gate

- exclusive-OR (XOR) gate

$$X \oplus Y = X Y' + X' Y$$

1 if only one variable is equal to 1, but not both

- exclusive-NOR gate

$$(X \oplus Y)' = X Y + X' Y'$$

1 if both are equal to 1 or both are equal to 0

- they are to be the complement of each other

## 2.7 Exclusive-OR Gate

- properties

$$X \oplus 0 = X$$

$$X \oplus 1 = X'$$

$$X \oplus X = 0$$

$$X \oplus X' = 1$$


$$X \oplus Y' = (X \oplus Y)'$$

$$X' \oplus Y = (X \oplus Y)'$$

$$A \oplus B = B \oplus A$$

$$(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$$

- implementation with NAND gates

 



## 2.8 Integrated Circuits

- Integrated Circuits (IC)
  - small silicon semiconductor crystal, called a chip
  - contains electronic components for the digital gates
  
- Levels of Integration
  - SSI (small scale integration),  $\leq 10$  gates
  - MSI, 10 ~ 100 gates
  - LSI, 100 ~ 1000s
  - VLSI, > 1000s



## 2.8 Integrated Circuits


- Digital Logic Families
  - RTL, DTL - earliest logic families
  - TTL - widespread, considered as standard
  - ECL - high speed operation
  - MOS - high component density
  - CMOS - low power consumption
  - BiCMOS - CMOS + TTL, used selectively
  
- Positive and Negative Logic
  - Normal Convention:
    - Positive Logic/Active High  
Low Voltage = 0; High Voltage = 1
  - Alternative Convention sometimes used:
    - Negative Logic/Active Low  
Low Voltage = 1; High Voltage = 0



## 2.8 Integrated Circuits

X	Y	Z
L	L	L
L	H	L
H	L	L
H	H	H


(a) Truth table with H and L

 

(b) Gate block diagram

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

(c) Truth table for positive logic

 

(d) Positive-logic AND gate

X	Y	Z
1	1	1
1	0	1
0	1	1
0	0	0

(e) Truth table for negative logic



(f) Negative-logic OR gate

(f) polarity indicator:  
small triangles in I/O